

# DIGITAL ALARM CLOCK

## ABSTRACT

Most people in the whole world use digital clocks with various functionalities. This is a technical report for this project - DIGITAL ALARM CLOCK. The proposed system will count the hour, minute, and second, along with 4 modes of operation like resetting and setting the time, setting alarm, changing hour format. The system was modeled in VHDL (Very-high-speed integrated circuit Hardware Description Language) in Quartus.

## ANALYSIS

 


Figure.1: Block diagram of the digital alarm clock

## Features

- Processes

Name	Type (filtered)	State	Order	Parent Path
line__69	VHDL Process	Wait	-	/tb_top
line__60	VHDL Process	Wait	-	/tb_top
PROCESS_out3	VHDL Process	Queued	-	/tb_top/dut
PROCESS_out2	VHDL Process	Queued	-	/tb_top/dut
PROCESS_out1	VHDL Process	Queued	-	/tb_top/dut
PROCESS_out0	VHDL Process	Queued	-	/tb_top/dut
PROCESS_ALARMSETTING	VHDL Process	Wait	-	/tb_top/dut
PROCESS_ALARMCOMPARE	VHDL Process	Queued	-	/tb_top/dut
PROCESS_ALARMONOFF	VHDL Process	Wait	-	/tb_top/dut
PROCESS_CHANGETIME	VHDL Process	Wait	-	/tb_top/dut
PROCESS_SELECT	VHDL Process	Wait	-	/tb_top/dut
PROCESS_CLK	VHDL Process	Queued	-	/tb_top/dut
PROCESS_MODE	VHDL Process	Wait	-	/tb_top/dut
PROCESS_FORMAT	VHDL Process	Wait	-	/tb_top/dut

- Four Operating Modes:
  - Mode Control - Using Q(4bit)** : It goes like 0001 -> 0010 -> 0100 -> 1000
  - Mode0 - Display Mode** : 7 segment decoders are used. The following is the behavior of the decoder. I have implemented the decoder at the algorithmic level:

```

-----display 7 SEG-----
PROCESS_m0 : PROCESS(r_m0, CLK) is
begin
  if (rising_edge(clk)) then
    r_m0 <= m0;
    if (Q = "0100") then
      r_m0 <= a_m0;
    elsif(alarmOut = "111111") then
      OUT_0 <= transport alarmOut after 60sec;
    end if;
    case r_m0 is
      when "0000" => OUT_0 <= "011111"; -- '0'
      when "0001" => OUT_0 <= "0000110"; -- '1'
      when "0010" => OUT_0 <= "1011011"; -- '2'
      when "0011" => OUT_0 <= "1001111"; -- '3'
      when "0100" => OUT_0 <= "1100110"; -- '4'
      when "0101" => OUT_0 <= "1101101"; -- '5'
      when "0110" => OUT_0 <= "1111101"; -- '6'
      when "0111" => OUT_0 <= "0000111"; -- '7'
      when "1000" => OUT_0 <= "1111111"; -- '8'
      when "1001" => OUT_0 <= "1101111"; -- '9'
      when "1010" => OUT_0 <= "1110111"; -- 'A'
      when "1011" => OUT_0 <= "1111100"; -- 'b'
      when "1100" => OUT_0 <= "1111001"; -- 'C'
      when "1101" => OUT_0 <= "1011110"; -- 'd'
      when "1110" => OUT_0 <= "1111001"; -- 'E'
      when "1111" => OUT_0 <= "1110001"; -- 'F'
      when others => NULL;
    end case;
  end if;
end PROCESS PROCESS_m0;

```

Figure.2: 7 segment decoder code of m0

- **Mode1 - Change hour format:** The default hour format of the project is 12h. We can change it to 24h or 12h using a converter. *T\_Format* is given as an internal signal which is triggered when we go to this mode.
- **Mode2 - SET alarm:** When Q = "0010", We can set alarm time at PROCESS\_ALARMSETTING. When current time reaches the alarm time, "alarmOut" convert "00000000" to "11111111" and 7 segment outputs FF:FF for 1 min. We can turn off the alarm using button "A" which change signal of "alarmOn" 1 to 0 also vice versa.
- **Mode3 - SET Current time:** We can change the time according to the time zone. With the help of UP and DOWN, the time can be adjusted.
- **RESET:** When reset the clock starts from 00:00 or 12 AM. And the alarm is set at 11:11.
- From the structural model of the clock in Figure.1, it is observed that we can embed the output of all the hour, minute, and second in 4-bit binary.
- Many FSM were analyzed to have the complete design. The UP and DOWN function values are stored and are given for display only when SET is high.
- The alarm set vector and time vectors of all hour bits and minute bits are compared. When all equal then the display vector values become "1111", making it display FF.

## SIMULATION RESULTS

 


Figure.5: Output waveform

## User Guide

- Reset: Time is set to 00:00 in 12h format and alarm is set to 11:11
- Mode:
  - Mode\_0: Display time
  - Mode\_1: Time format change, you can change the format by changing C(additional input)
  - Mode\_2: Set alarm using UP and DOWN. At this time you can see the alarm time to set in the display and using B(additional input) you can select the set(hour 00~24 or 12~00 /min 00~59~00) to change.
  - Mode\_3: Set time. Similarly, here change the time to set using UP and DOWN. The display will show the time to set during this mode.
- UP/DOWN: To set the time and alarm.
- A: The user can set the alarm off by keeping A high('1').
- B: This is for set selection. It goes like *minute -> hour*
- C: This is for changing the Time format when in Mode\_2.

## CONCLUSION

In this project, I have implemented a digital clock with an alarm using VHDL in Quartus. I learned more fundamental principles of designing digital systems. The digital clock can be reset and we can adjust the time according to different time zones too. It has 4 displays that make it user-friendly.

## REFERENCES

- [1] Oyewale Ademola S., '*Digital Alarm Clock SIWES 300 Project*', GRID LABORATORY, OBAFEMI AWOLOWO UNIVERSITY ILE-IFE
- [2] Tesfamichael Molla, '*Digital Clock Project*', Technical Report · January 2017  
DOI: 10.13140/RG.2.2.27401.90724
- [3] <https://vhdlguru.blogspot.com/2010/03/digital-clock-in-vhdl.html>
- [4] <https://electronics-course.com/digital-clock#hide>
- [5] <https://www.fpga4student.com/2016/11/vhdl-code-for-digital-clock-on-fpga.html>